

Terminal Names in IBIS Buffer Graphics C_comp to ?

Walter Katz

SiSoft


IBIS ATM

May 19, 2015

Outline / Conclusions


- Using IBIS Terminator Model to Illustrate the Issues
- IBIS Should Use Consistent Model Terminal Names
- Voltages at Terminals are Always Referenced to GND
- GND is a Simulator Reference Node (often Node 0)
- GND Should Not Be Confused with IBIS-ISS Reserved Node GND
- External Model Terminal (Port) A_gnd Should Not Be Used If Doing Power Aware Simulations Since There is No Way to Make a Connection From This Terminal to a Component Pin
- Should Not Confuse IBIS Model Terminals With Voltages Used to Derive IV Curves
- C_comp_* is Preferred Over C_comp for Power Aware Simulations

The Terminator Model in IBIS 5.1/6.0

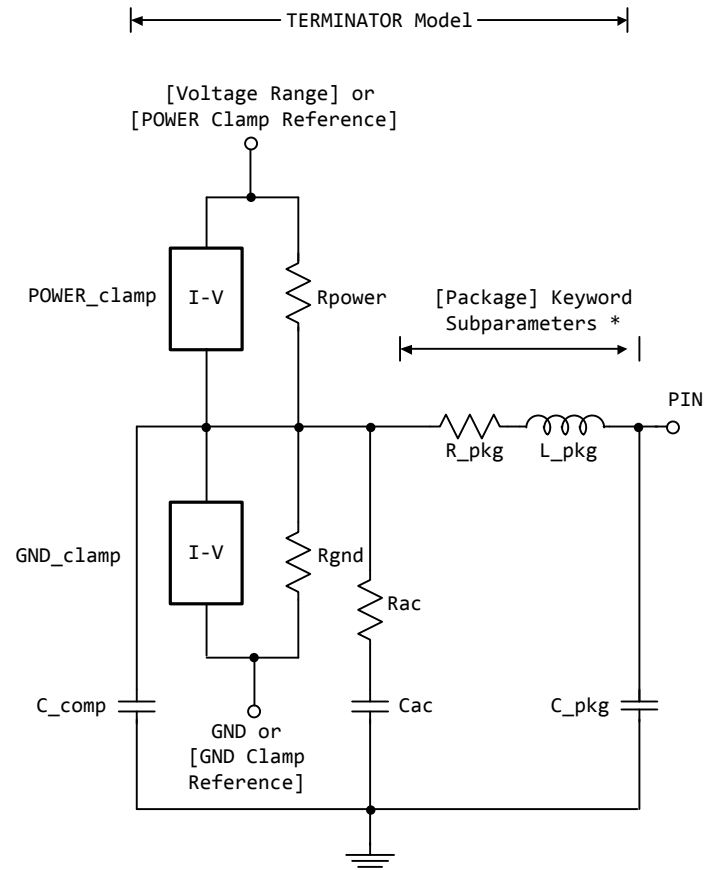

* Note: More advanced package parameters are available within this standard, including more detailed power and ground net descriptions.


The Terminator Model in IBIS 5.0

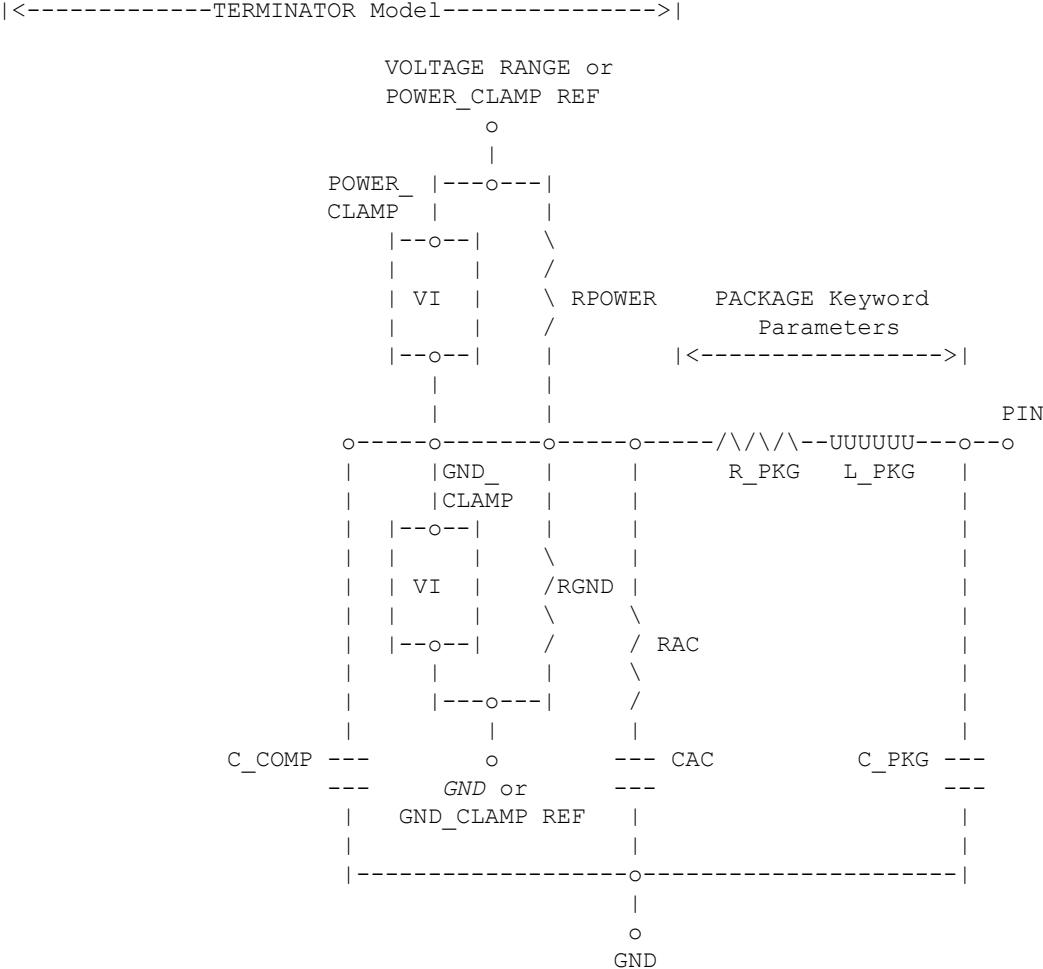

Terminals Should Be Named A_pcref and A_gcref

```
|<-----TERMINATOR Model----->|
```

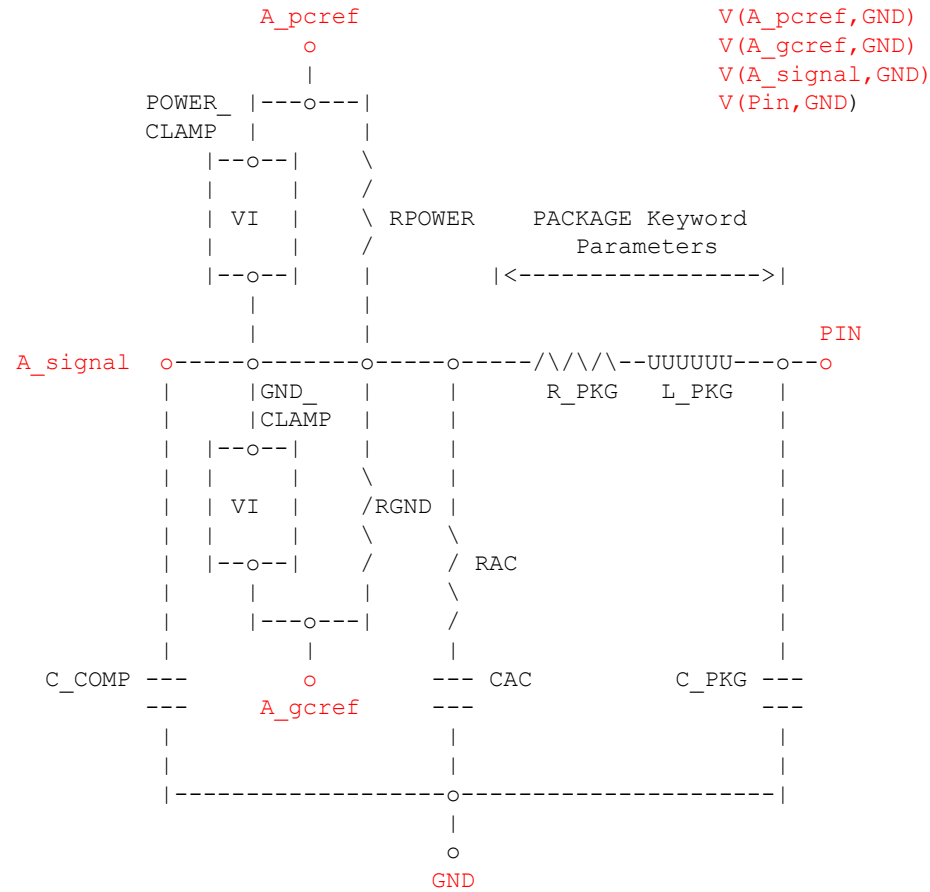The Voltages at terminals A_pcref, A_Signal, A_gcref and node PIN are referenced to GND



IBIS Model Terminals That Need to Connect to Package Models

Discussed in This Presentation

- A_signal
- A_puref
- A_pcref
- A_pdref
- A_gcref

Like Ones on Left

- A_pos
- A_neg
- A_signal_pos
- A_signal_neg

[External Model Only]

- A_extref

No Way to Connect to Package

- A_gnd

Terminal Connections To IV Curves

- [Ground Clamp] IV
 - Current from $(A_{\text{signal}} - A_{\text{gcref}})$
 - Derivation Conditions
 - A_{gcref} = [GND Clamp Reference] referenced to GND
 - A_{signal} referenced to GND
- [Power Clamp] IV
 - Current from $(A_{\text{pcref}} - A_{\text{signal}})$
 - Derivation Conditions
 - A_{pcref} = [Power Clamp Reference] referenced to GND
 - A_{signal} referenced to GND

Terminal Connections To IV Curves (cont)

- [Pulldown] IV
 - Current from $(A_{\text{signal}} - A_{\text{pcref}})$
 - Derivation Conditions
 - A_{pcref} = [Pulldown Reference] referenced to GND
 - A_{signal} referenced to GND
- [Pullup Clamp] IV
 - Current from $(A_{\text{puref}} - A_{\text{signal}})$
 - Derivation Conditions
 - A_{puref} = [Pullup Reference] referenced to GND
 - A_{signal} referenced to GND

Derivation Voltage Precedence

- [Pullup Reference]
 - [Pullup Reference] parameter
 - [Voltage Range] parameter
- [Power Clamp Reference]
 - [Power Clamp Reference] parameter
 - [Voltage Range] parameter
- [Pulldown Reference]
 - [Pulldown Reference] parameter
 - 0.0
- [GND Clamp Reference]
 - [GND Clamp Reference] parameter
 - 0.0

What Should C_comp Connect To?

1. Correct power aware model should use
 - C_comp_power_clamp
 - C_comp_gnd_clamp
2. C_comp to GND (Simulator Reference Node e.g. Node 0)
3. C_comp to A_gcref
4. C_comp split between A_gcref and A_pcref

Which is worst of three evils (2, 3, 4)?

1. C_comp to local ground
2. C_comp split arbitrarily between local ground and local power
3. C_comp to some “simulator/chassis” ground far, far away.

Does it Matter? Will simulation results change if rail voltages are constant?