

EMD Differential Transmission Line Model Rev 1.0

Walter Katz
June 17, 2008

Subckt Elements

- R Resistor
- L Inductor
- C Capacitor
- G Conductance
- K Element
- T Tline
- W Line
 - RLGC
 - Table Driven
- S parameter element
- Controlled Sources
- V DC Voltage
- X Subckt
- Other possible elements
 - Impulse Response
 - Poles and Zeros
- Miscellaneous
 - .include
 - .parameter
- Corner
 - Slow/Typ/Fast
 - Min/Max Noise
 - Min/Max CrossTalk

Assumption

Reference Nodes is perfect Ground at both ends of Differential Transmission Line

Length is 1"

Nodes are D.H, D.L, P.H, P.L

- D Die side**
- P Package Side**
- H Active High**
- L Active Low**

Physical Description

**Stripline
Length
Er
Conductivity
Loss tangent
Surface roughness
Dielectric Thickness
Trace height above plane
Trace widths
Trace thickness
Trapezoidal shape
Trace separation**

Physical/Electrical Description

Length

Zodd

Zeven

Er

Conductivity

Loss tangent

Surface roughness

Trace widths

Trace thickness

Lumped Model

C_D.H	D.H	0	C=<capacitance>
R_H	D.H	H	R=<resistance>
L_H	P.H	H	L=<inductance>
C_P.H	P.H	0	C=<capacitance>
C_D.L	D.L	0	C=<capacitance>
R_L	D.L	L	R=<resistance>
L_L	P.L	L	L=<inductance>
C_P.L	P.L	0	C=<capacitance>

Coupled Lumped Model

```
C_D.H D.H 0    C=<capacitance>
R_H     D.H H    R=<resistance>
L_H     P.H H    L=<inductance>
C_P.H P.H 0    C=<capacitance>
C_D.L D.L 0    C=<capacitance>
R_L     D.L L    R=<resistance>
L_L     P.L L    L=<inductance>
C_P.L P.L 0    C=<capacitance>
KL     L_H L_L K=<coupling>
C_D     D.H D.L C=<capacitance>
C_P     P.H P.L C=<capacitance>
```

Lossless Uncoupled Tlines

```
TH D.H P.H Td=<delay> Zo=<impedance>
TL D.L P.L Td=<delay> Zo=<impedance>
```

Other Model Formats

Other D.H D.L P.H P.L L=.0254	RLGCmodel=<RLGCmodel>
Other D.H D.L P.H P.L L=.0254	TABLEmodel=<TABLEmodel>
Other D.H D.L P.H P.L	TouchstoneFile=<file>.s4p
Other D.H D.L P.H P.L	ImpulseFile=<file>.i4p
Other D.H D.L P.H P.L	PoleZeroModel=<PoleZeroModel>
Other D.H D.L P.H P.L	LadderModel=<LadderModel>
Other D.H D.L P.H P.L	?=<?>

RLGC Models

RLGCmodel

Lo Co Ro Go Rs Gd

Proprietary?

Accurate and concise representation of frequency dependence

TABLEmodel

RIMODEL

CMODEL

LMODEL

GMODEL

ICM is same as **TABLEmodel** except supports lumped and sparse

Resistance

Capacitance

Inductance

Conductance

Touchstone File

Touchstone 1.0 is all that is required

The person creating the EMD model “knows” how the s4p was generated, and therefore knows how to associate the nodes of the differential pair with the ports of the s4p data

If model was NNFF then

Other D.H D.L P.H P.L TouchstoneFile=<file>.s4p

If model was NFNF then

Other D.H P.H D.L P.L TouchstoneFile=<file>.s4p

Touchstone 2.0 can save 2x disc space for sNp where N >4

Sparse Touchstone representation will be required for large coupled systems