




Quiet line experiment

IBIS Open Forum Teleconference

October 7, 2005

Arpad Muranyi
Signal Integrity Engineering
Intel Corporation
arpad.muranyi@intel.com

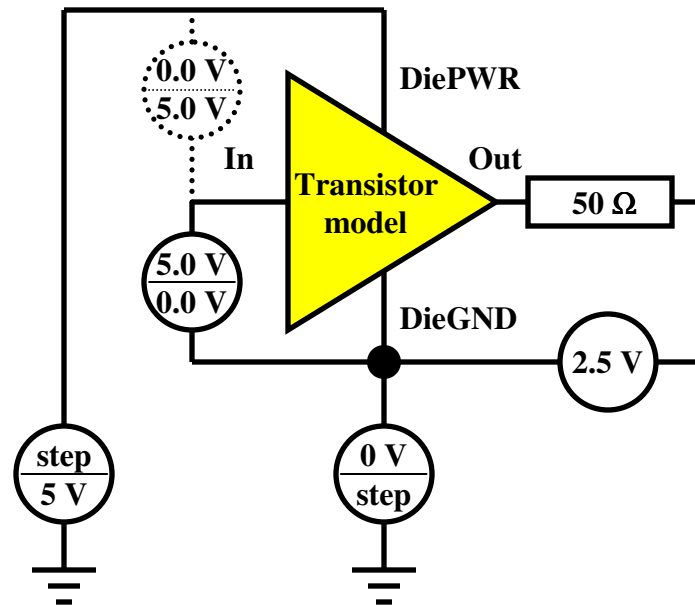
Simulation circuit using ‘IBIS class’ transistor model




HSPICE simulation file

```
Testing Output Response to Supply Noise
*****
.OPTIONS POST=1 POST_VERSION=9007 PROBE ACCURATE RMAX=0.5
.TRAN 1.0ps 4.0ns SWEEP Tpoint LIN 10 101e-12 1001e-12
.LIB 'Process.lib' Typ
*****
.PROBE
+ DiePWR = V(DiePWR,DieGND)
+ DieGND = V(DieGND)
+ Out = V(Out,DieGND)
*****
.param Tpoint = 101ps
*
*Vvcc DiePWR 0 DC= 5.0
Vvcc DiePWR 0 PWL
+ 0.0 5.0
+ 0.1ns 5.0
+ Tpoint 4.0
+ 10.0ns 4.0
*
Vgnd DieGND 0 DC= 0.0
*Vgnd DieGND 0 PWL
*+ 0.0 0.0
*+ 0.1ns 0.0
*+ Tpoint 1.0
*+ 10.0ns 1.0
*
Vin In DieGND DC= 5.0
*Vin DiePWR In DC= 0.0
*****
X0 In Out DiePWR DiePWR DieGND DieGND DieGND IO_buf
* in out pu pc pd gc en
*
Rload Out Vtt R= 50.0
Vload Vtt DieGND DC= 2.5
*****
.END
*****
```

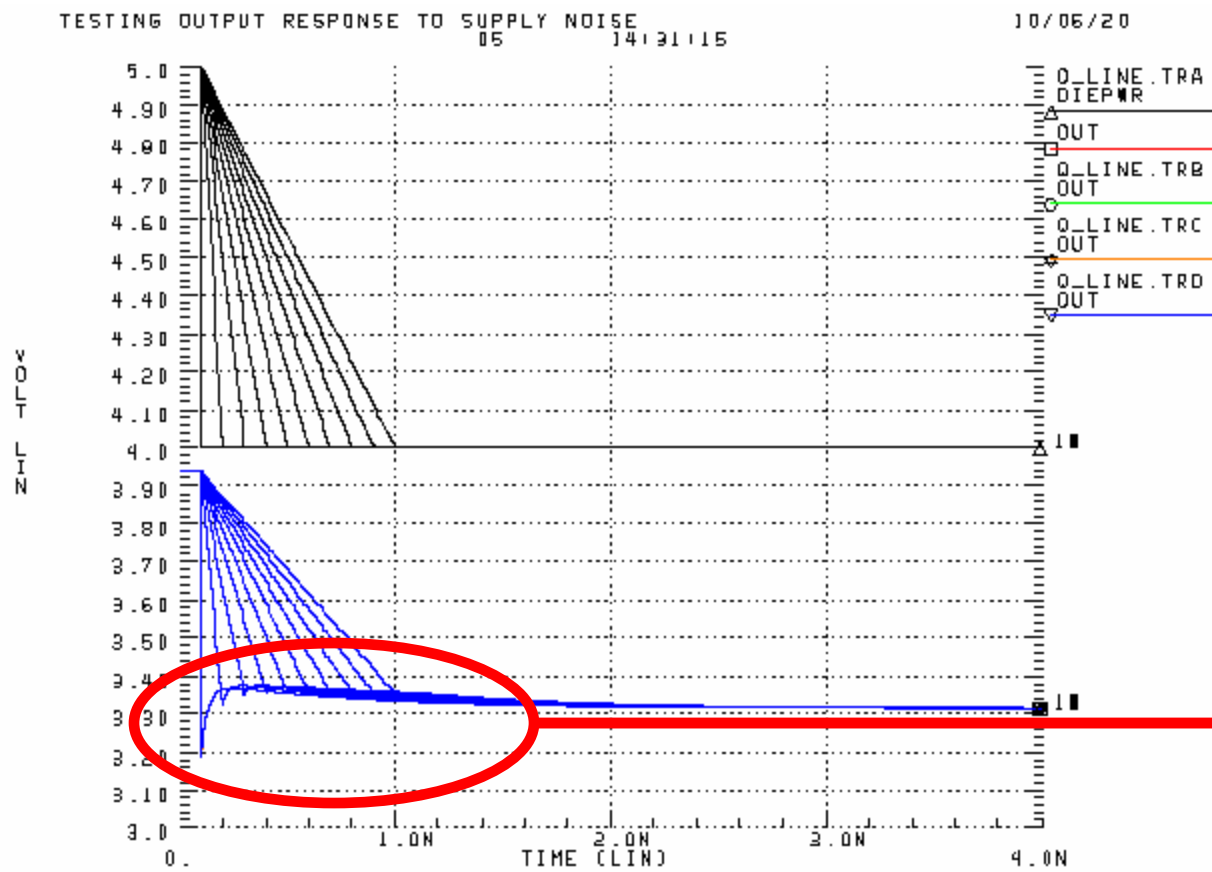The four configurations give identical results (high state)



Zooming in to see the details...

 


Make the PU and PD asymmetric

```
*****
.SUBCKT IO_buf d_in pad DiePWR p_clamp DieGND g_clamp enable
*****
X1 enable en_b DiePWR DieGND INVERTER
X2 d_in en_b pre_p1 DiePWR DieGND NAND2
X3 d_in enable pre_n1 DiePWR DieGND NOR2
X4 pre_p1 pre_p2 DiePWR DieGND INVERTER mult_p=2 mult_n=2
X5 pre_n1 pre_n2 DiePWR DieGND INVERTER mult_p=2 mult_n=2
X6 pre_p2 pre_p2 gate_p DiePWR DieGND NAND2 mult_p=4 mult_n=2
X7 pre_n2 pre_n2 gate_n DiePWR DieGND NOR2 mult_p=2 mult_n=4
*
Mp pad gate_p DiePWR p_clamp PMOS L=0.800U W=43.40U NRD=0.0897 NRS=0.0737
+ AS=434.0P AD=217.0P PS=106.8U PD=53.40U
+ M=12
Mn pad gate_n DieGND g_clamp NMOS L=0.800U W=43.40U NRD=0.0897 NRS=0.0714
+ AS=434.0P AD=217.0P PS=106.8U PD=53.40U
+ M=6
*
*C1 pre_p2 DieGND C=0.07pF
*C2 pre_n2 DieGND C=0.07pF
*C3 gate_p DieGND C=0.04pF
*C4 gate_n DieGND C=0.03pF
*
R1 pad rcv_in R=200
*C5 rcv_in DieGND C=0.2pF
X8 rcv_in rcv_out DiePWR DieGND INVERTER
*
```


**Chaged to M=6
to make PU and
PD asymmetric**

Adding or removing these capacitors doesn't make the agreement between the four conditions any weaker

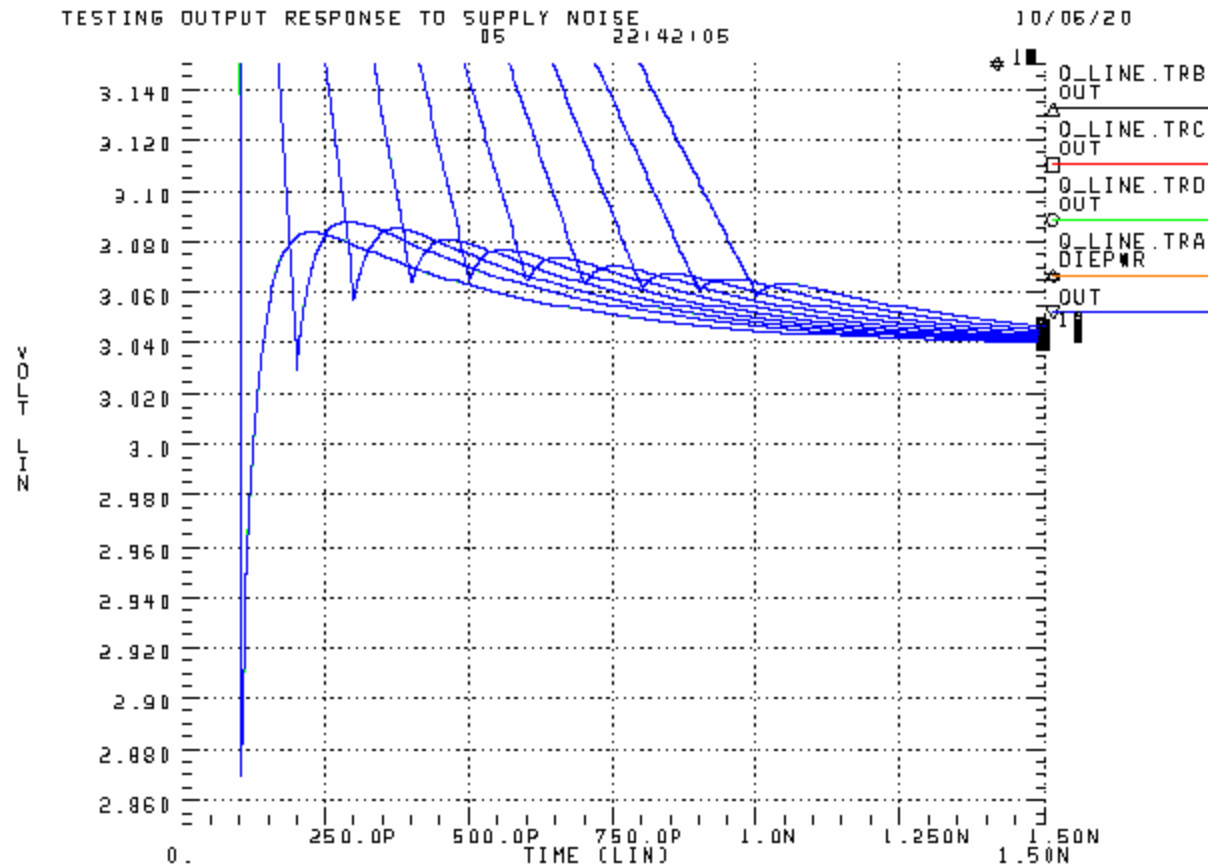
PU reduced to half the strength - High state




Gate voltage of the output transistors

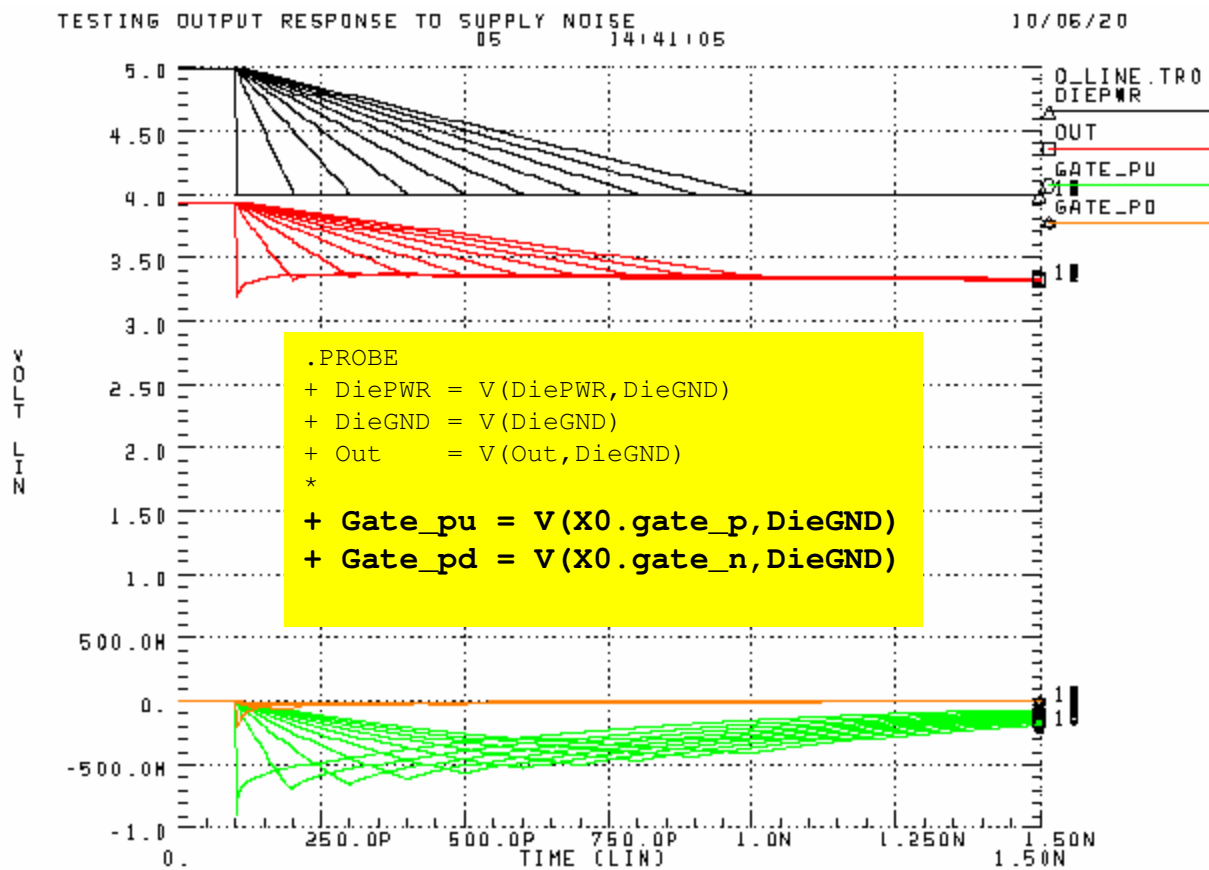


Zooming in to see the details...

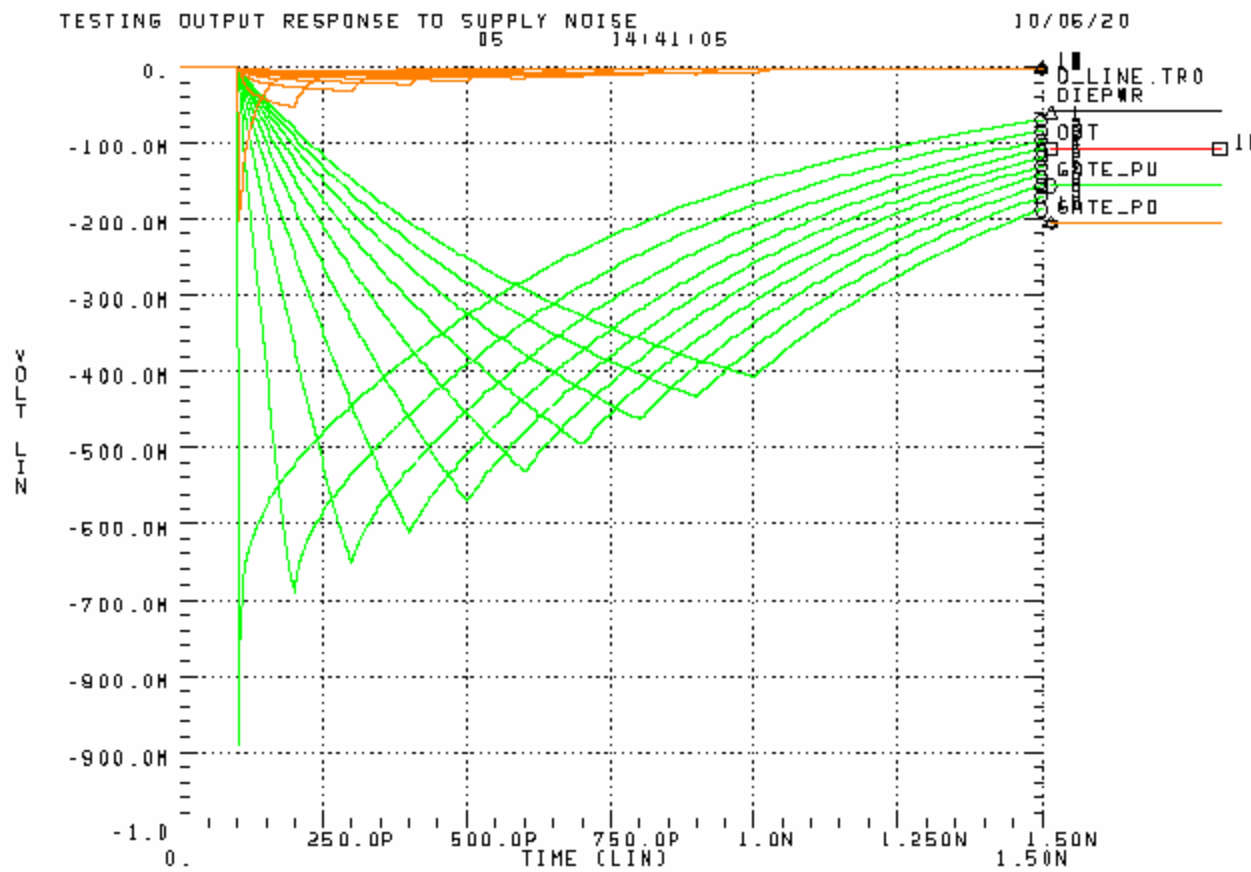

 
The four configurations give identical results (low state)




Zooming in to see the details...

 

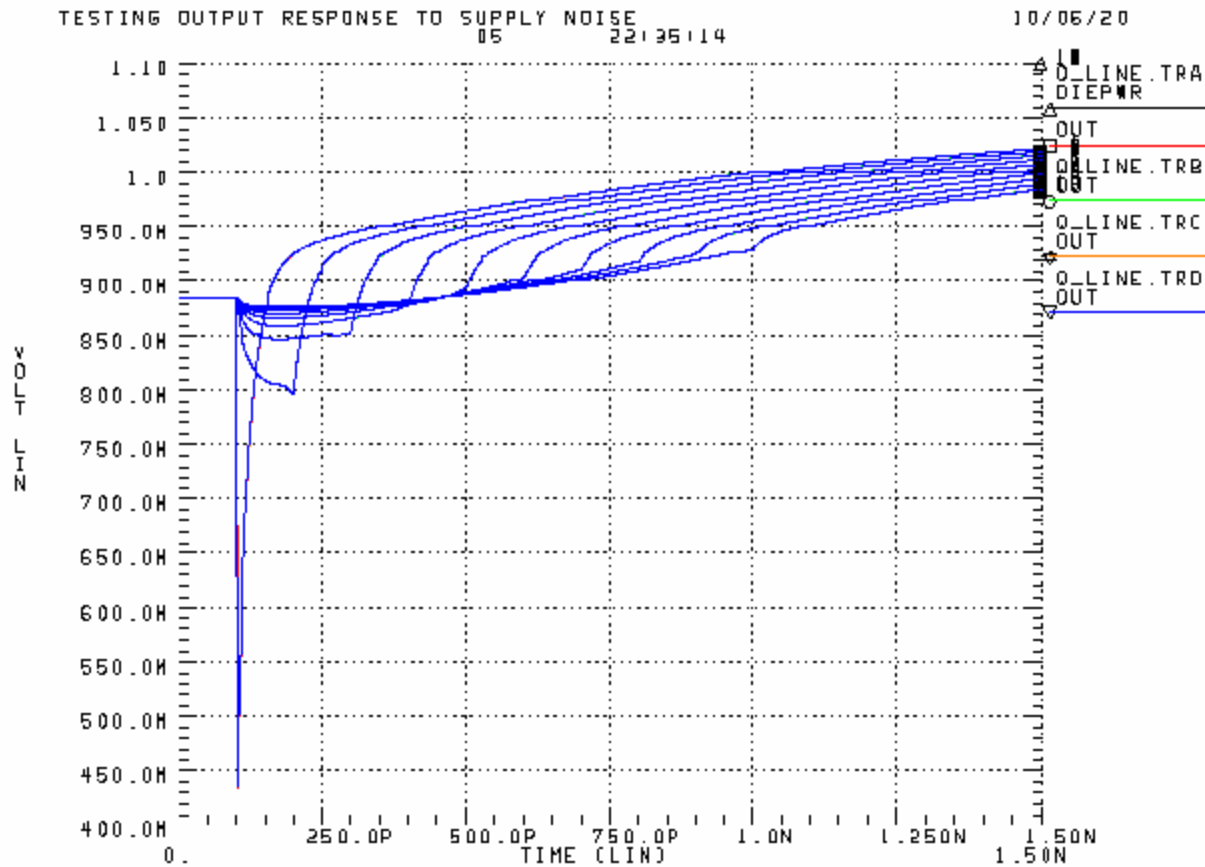
PU reduced to half the strength - Low state



Gate voltage of the output transistors

 

Zooming in to see the details...

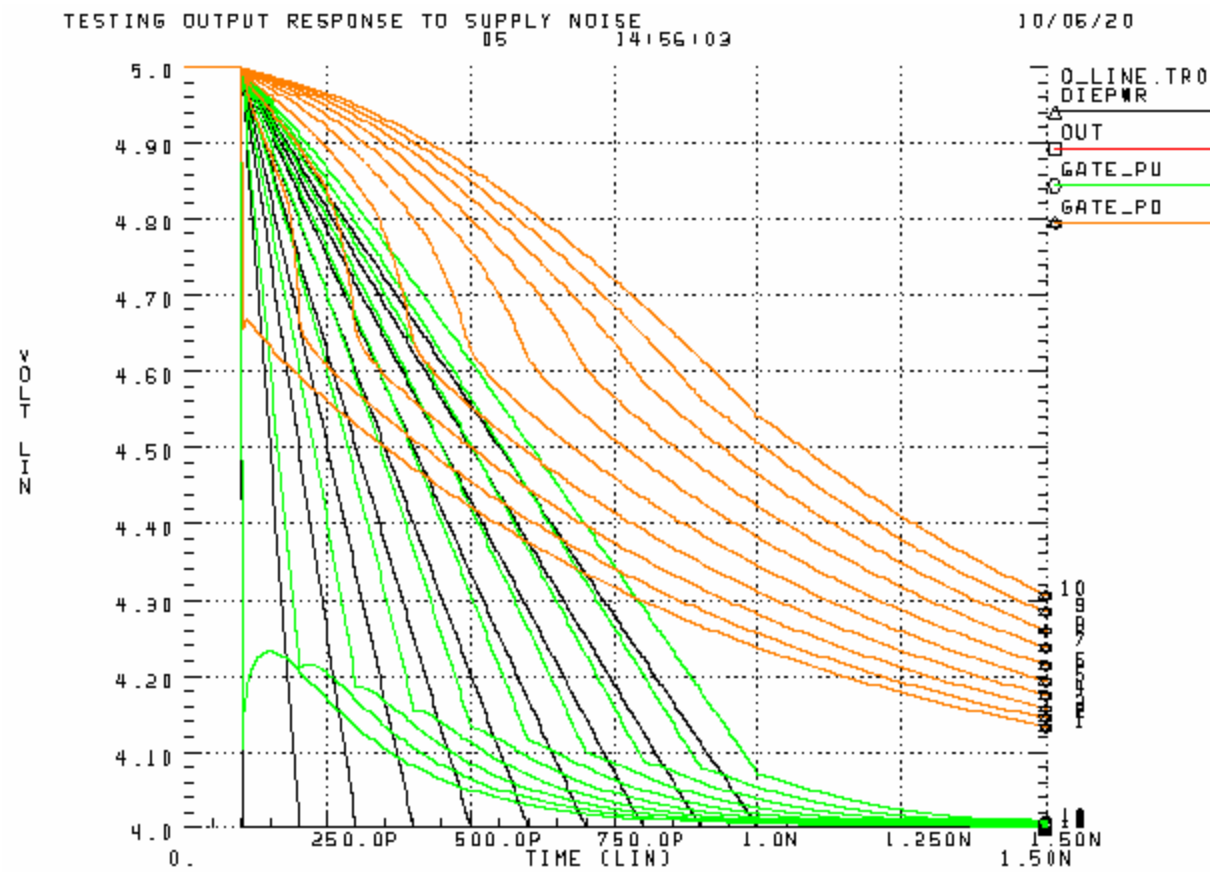

Conclusions

- Whether we are modulating the top or bottom supply voltage **DOES NOT MATTER**
- Due to internal RC effects the gate voltage of the output transistors will not be able to follow rapid supply voltage variations instantaneously
- The gate modulation effect cannot be modeled by DC measurements alone
- We have to find a good way to describe these AC effects in a general way before BIRD97/98 can be completed