



Time-Domain Extraction and SPICE Macromodeling

Bob Ross, Teraspeed Labs, USA
bob@teraspeedlabs.com

DesignCon IBIS Summit
(after DesignCon 2022)
Santa Clara, California and Virtual
April 8, 2022



Previous Presentations

- “Time-Domain Macromodel Extraction” (briefly)
www.ibis.org/summits/may21/ross1.pdf
 - Nomenclature and some mathematical identities
 - Duality (see presentation for details)
 - Key equation for steepest descent optimization
 - Laplace transform optimization flow for simultaneous numerator and denominator coefficients
 - Last column mathematics for a companion matrices (not shown here)
 - In place algorithms (mentioned)
 - Constraints



Previous Presentations (continued)

- “SPICE Macromodel Generation”
www.ibis.org/summits/may21/ross2.pdf
 - Mostly included here
 - Main point is to illustrate a set of circuits (and their efficiencies) for generating poles and zeros
 - Pole/zero cancellation is illustrated
 - Cascaded circuits were common practice in operational amplifier data book/sheet models



TIME-DOMAIN EXTRACTION

- Goal – Low-order Laplace transform network function from time-domain measurements (or simulations) as a ratio of polynomials in s
 - Noisy measurements
 - Uncoupled networks
 - Least squared error steepest descent algorithm
- Show some not so well-known mathematical identities
 - Duality
 - Last column mathematics for functions of companion matrices
 - In place algorithms
- Based on original correspondence 1969 – 1972 with Janez Valand (Yugoslavia/Croatia) and actual product implementation (1990's)
- Derivations and proofs not shown
 - Proofs based on power series expansions and companion matrix relationships



Special Notation - Equations

Laplace Transform

$$X(s) = \frac{a_{n-1}s^{n-1} + \dots + a_0}{s^n + b_{n-1}s^{n-1} + \dots + b_0},$$

Differential Equation

$$x^n(t) + b_{n-1}x^{n-1}(t) + \dots + b_0x(t) = 0$$

initial conditions, $x(0), \dots, x^{n-1}(0)$,

Difference Equation

$$x_n(t) + d_{n-1}x_{n-1}(t) + \dots + d_0x_0(t) = 0$$


initial conditions, $x_0(0), \dots, x_{n-1}(0)$,

Z Transform

$$Z(z) = \frac{z(c_{n-1}z^{n-1} + \dots + c_0)}{z^n + d_{n-1}z^{n-1} + \dots + d_0}.$$



Conversions and Responses

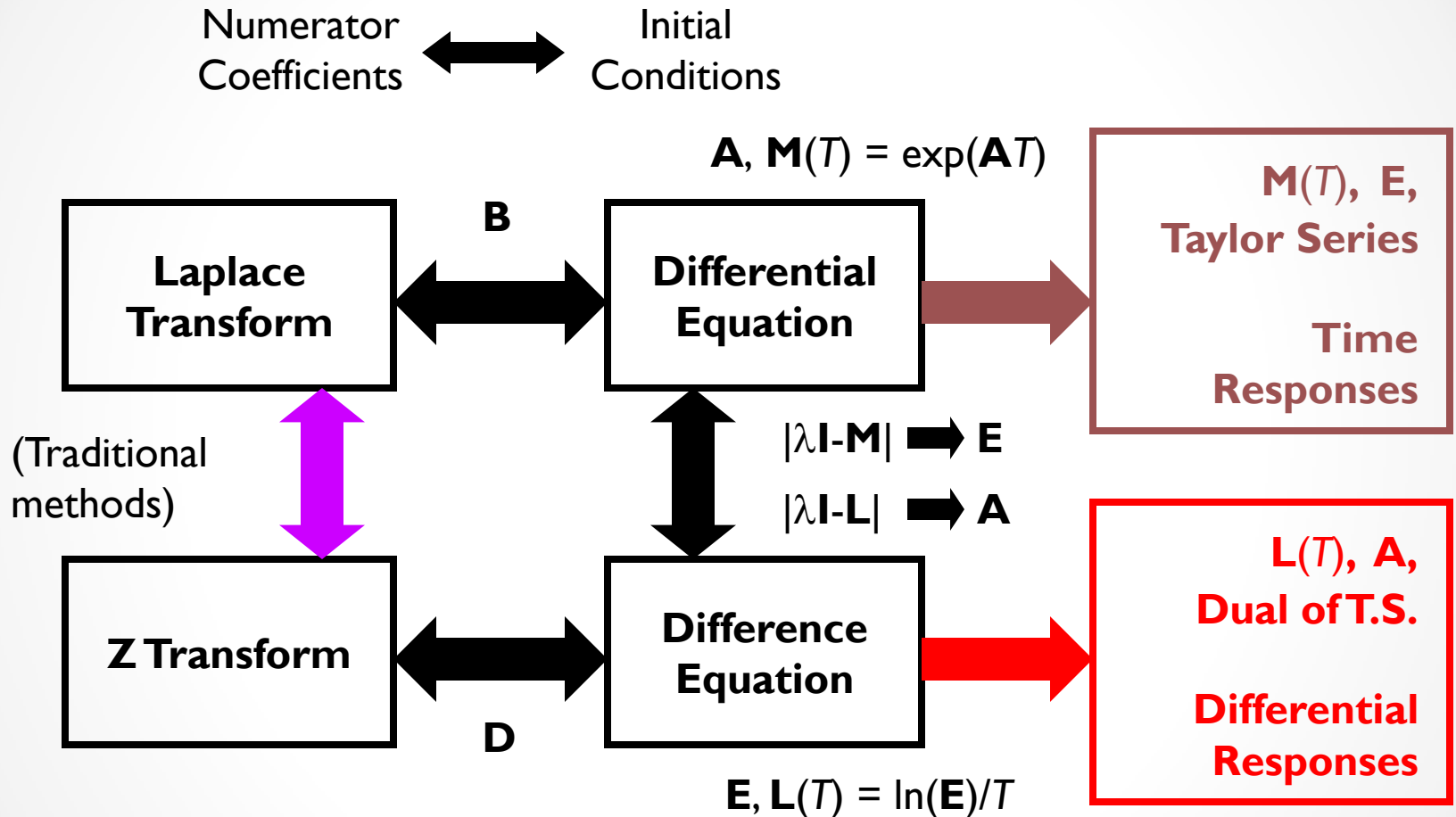

Differential Equations

$$dx(t)/dt = \mathbf{A}x(t)$$

$$\mathbf{A} = \begin{bmatrix} 0 & 1 & \cdots & 0 \\ 0 & 0 & \cdots & 0 \\ \vdots & \vdots & & \vdots \\ 0 & 0 & \cdots & 1 \\ -b_0 & -b_1 & \cdots & -b_{n-1} \end{bmatrix}$$

$$\mathbf{x}(t+T) = \mathbf{M}\mathbf{x}(t)$$

$$\mathbf{M} = \exp(\mathbf{A}T)$$

Companion Matrices

Difference Equations

$$\mathbf{z}(t+T) = \mathbf{E}\mathbf{z}(t)$$

$$\mathbf{E} = \begin{bmatrix} 0 & 1 & \cdots & 0 \\ 0 & 0 & \cdots & 0 \\ \vdots & \vdots & & \vdots \\ 0 & 0 & \cdots & 1 \\ -d_0 & -d_1 & \cdots & -d_{n-1} \end{bmatrix}$$

$$dz(t)/dt = \mathbf{L}z(t)$$

$$\mathbf{E} = \exp(\mathbf{L}T)$$

$$\mathbf{L} = \ln(\mathbf{E})/T$$



Differential Equations

$$\mathbf{x}(t) = [x^0(t), x^1(t), \dots, x^{n-1}(t)]^T,$$

$$\mathbf{a} = [a_{n-1}, \dots, a_0]^T,$$

$$\mathbf{B} = \begin{bmatrix} 1 & 0 & \dots & 0 & 0 \\ b_{n-1} & 1 & \dots & 0 & 0 \\ \vdots & \vdots & \ddots & \vdots & \vdots \\ b_2 & b_3 & \dots & 1 & 0 \\ b_1 & b_2 & \dots & b_{n-1} & 1 \end{bmatrix}$$

$$\mathbf{a} = \mathbf{B}\mathbf{x}(0)$$

Difference Equations

$$\mathbf{z}(t) = [x_0(t), x_1(t), \dots, x_{n-1}(t)]^T$$

$$\mathbf{c} = [c_{n-1}, \dots, c_0]^T$$

$$\mathbf{D} = \begin{bmatrix} 1 & 0 & \dots & 0 & 0 \\ d_{n-1} & 1 & \dots & 0 & 0 \\ \vdots & \vdots & \ddots & \vdots & \vdots \\ d_2 & d_3 & \dots & 1 & 0 \\ d_1 & d_2 & \dots & d_{n-1} & 1 \end{bmatrix}$$

$$\mathbf{c} = \mathbf{D}\mathbf{z}(0)$$



Recursive Taylor Series

(Repeat b and c)

a) Initialize: $i = 1, \dots, n-1$

$$x(0) = a_{n-1} \quad x^i(0) = a_{n-1-i} - \sum_{j=0}^{i-1} b_{n-i-j} x^j(0)$$

b) Extend: $i = n, \dots, p$

$$x^i(t) = - \sum_{j=0}^{n-1} b_j x^{i-n-j}(t)$$

c) Next time step: $i = 0, \dots, n-1$ (Taylor series)

$$x^i(t+T) = \sum_{j=i}^p x^j(t) \frac{T^{j-i}}{(j-i)!}$$

R. I. Ross, "Evaluating the Transient Response of a Network Function," *Proc. IEEE*, vol.55, pp. 615-616, May 1967



Differential

Eq'n Sensitivities

$$\left[\frac{\partial x(t)}{\partial a_0}, \frac{\partial x(t)}{\partial a_1}, \dots, \frac{\partial x(t)}{\partial a_{n-1}} \right]^T =$$

$$\left[\frac{\partial x(t)}{\partial a_0}, \frac{\partial x^1(t)}{\partial a_0}, \dots, \frac{\partial x^{n-1}(t)}{\partial a_0} \right]^T$$

$$\left[\frac{\partial x(t)}{\partial b_0}, \frac{\partial x(t)}{\partial b_1}, \dots, \frac{\partial x(t)}{\partial b_{n-1}} \right]^T =$$

$$\left[\frac{\partial x(t)}{\partial b_0}, \frac{\partial x^1(t)}{\partial b_0}, \dots, \frac{\partial x^{n-1}(t)}{\partial b_0} \right]^T$$

$$\frac{\partial x^i(t)}{\partial a_j \partial b_k} = \frac{\partial x^{i+j+k}(t)}{\partial a_0 \partial b_0}$$

Difference

Eq'n Sensitivities

$$\left[\frac{\partial x(t)}{\partial c_0}, \frac{\partial x(t)}{\partial c_1}, \dots, \frac{\partial x(t)}{\partial c_{n-1}} \right]^T =$$

$$\left[\frac{\partial x(t)}{\partial c_0}, \frac{\partial x_1(t)}{\partial c_0}, \dots, \frac{\partial x_{n-1}(t)}{\partial c_0} \right]^T$$

$$\left[\frac{\partial x(t)}{\partial d_0}, \frac{\partial x(t)}{\partial d_1}, \dots, \frac{\partial x(t)}{\partial d_{n-1}} \right]^T =$$

$$\left[\frac{\partial x(t)}{\partial d_0}, \frac{\partial x_1(t)}{\partial d_0}, \dots, \frac{\partial x_{n-1}(t)}{\partial d_0} \right]^T$$


$$x_j(t) = x(t + jT), \quad j = 0, \dots, n-1$$

$$\frac{\partial x_i(t)}{\partial c_j \partial d_k} = \frac{\partial x_{i+j+k}(t)}{\partial c_0 \partial d_0}$$



Laplace Transform Extraction (T.S.)

Expanded on next slide

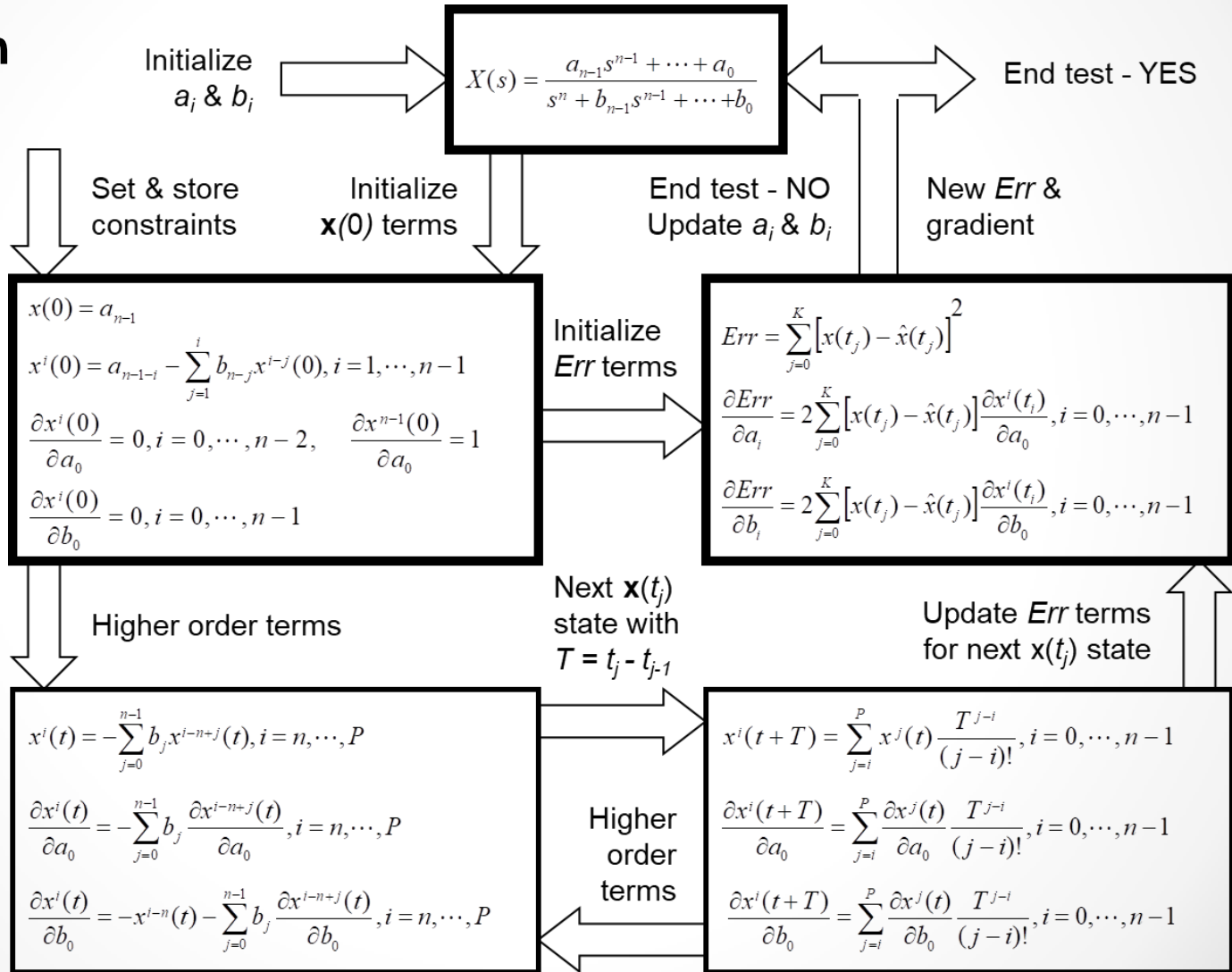

Initialize a_i & b_i

$$X(s) = \frac{a_{n-1}s^{n-1} + \dots + a_0}{s^n + b_{n-1}s^{n-1} + \dots + b_0}$$

End test - YES

Set & store constraints

Initialize $x(0)$ terms

End test - NO
Update a_i & b_i

New *Err* & gradient

$$x(0) = a_{n-1}$$

$$x^i(0) = a_{n-1-i} - \sum_{j=1}^i b_{n-j} x^{i-j}(0), i = 1, \dots, n-1$$

$$\frac{\partial x^i(0)}{\partial a_0} = 0, i = 0, \dots, n-2, \quad \frac{\partial x^{n-1}(0)}{\partial a_0} = 1$$

$$\frac{\partial x^i(0)}{\partial b_0} = 0, i = 0, \dots, n-1$$

Initialize *Err* terms

$$Err = \sum_{j=0}^K [x(t_j) - \hat{x}(t_j)]^2$$

$$\frac{\partial Err}{\partial a_i} = 2 \sum_{j=0}^K [x(t_j) - \hat{x}(t_j)] \frac{\partial x^i(t_j)}{\partial a_0}, i = 0, \dots, n-1$$

$$\frac{\partial Err}{\partial b_i} = 2 \sum_{j=0}^K [x(t_j) - \hat{x}(t_j)] \frac{\partial x^i(t_j)}{\partial b_0}, i = 0, \dots, n-1$$

Higher order terms

Next $x(t_j)$ state with $T = t_j - t_{j-1}$

Update *Err* terms for next $x(t_j)$ state

$$x^i(t) = -\sum_{j=0}^{n-1} b_j x^{i-n+j}(t), i = n, \dots, P$$

$$\frac{\partial x^i(t)}{\partial a_0} = -\sum_{j=0}^{n-1} b_j \frac{\partial x^{i-n+j}(t)}{\partial a_0}, i = n, \dots, P$$

$$\frac{\partial x^i(t)}{\partial b_0} = -x^{i-n}(t) - \sum_{j=0}^{n-1} b_j \frac{\partial x^{i-n+j}(t)}{\partial b_0}, i = n, \dots, P$$

Higher order terms

$$x^i(t+T) = \sum_{j=i}^P x^j(t) \frac{T^{j-i}}{(j-i)!}, i = 0, \dots, n-1$$

$$\frac{\partial x^i(t+T)}{\partial a_0} = \sum_{j=i}^P \frac{\partial x^j(t)}{\partial a_0} \frac{T^{j-i}}{(j-i)!}, i = 0, \dots, n-1$$



$$\frac{\partial x^i(t+T)}{\partial b_0} = \sum_{j=i}^P \frac{\partial x^j(t)}{\partial b_0} \frac{T^{j-i}}{(j-i)!}, i = 0, \dots, n-1$$

Available Constraints



- Denominator degree (number of poles)
- Ideal step response ($b_0=0.0$)
- Numerator degree (number of zeros, where lower degree produces less leading edge ripple)
- Set t_s start value, DC offset (y_0)
- Minimum and maximum frequencies for log frequency domain plots
- Initial value
- Final value



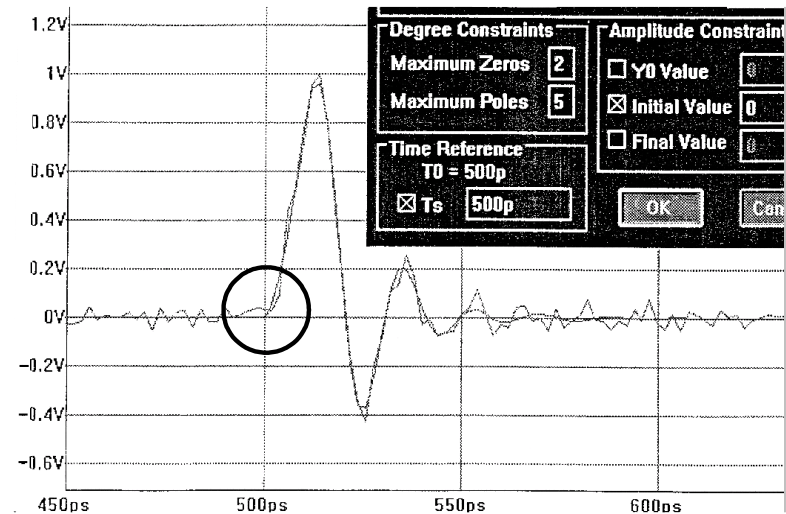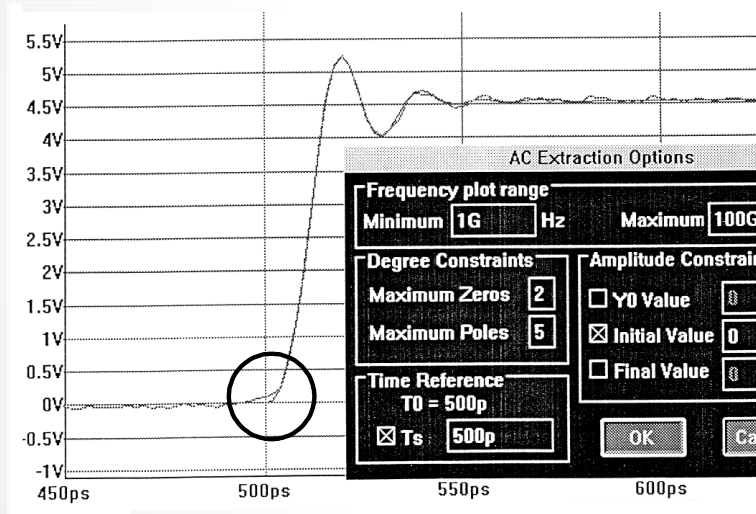Constraints (Oscilloscope Step and Impulse Response Extractions)



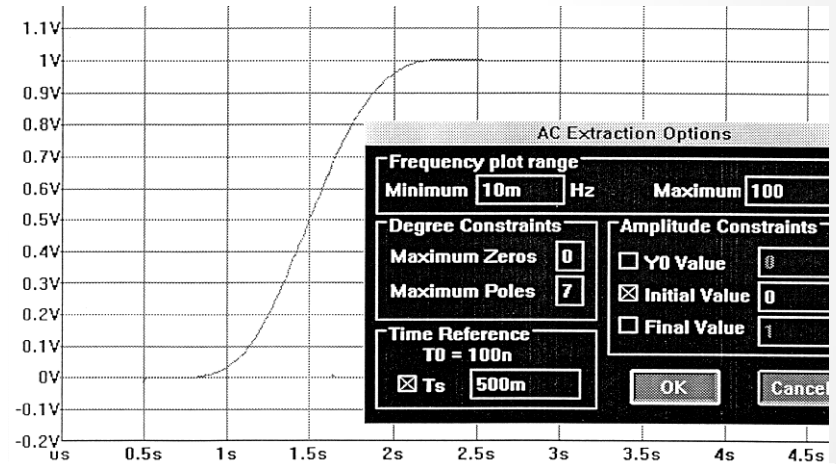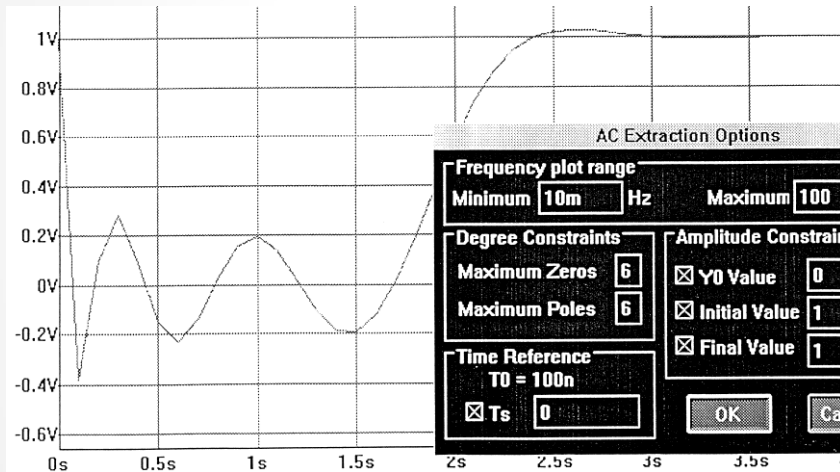Constraints – Maximally Flat Envelope Delay Networks



Conclusions

- Early (1970's) algorithm outlined for physical measurement-based time-domain extraction
- Most calculations done in place to save memory
- Most calculations used last-column matrix mathematics
- Many subroutines worked in both the difference equation and differential equation domains
- Laplace transform formulation allowed practical constraints to be implemented
- Result was a Laplace transform polynomial ratio, $N(s)/D(s)$, from a time-domain response



GENERATING SPICE MACROMODELS

- Preliminary material
- Macromodel references
- Networks for poles and zeros (and their efficiencies)
- Operational amplifier open-loop response
- Operational amplifier macromodel example
- Conclusion



Automatic Implementation

- Starting point – Laplace transform $H(s) = N(s)/D(s)$ as ratio of polynomials is s
- Laplace transform, pole/zero, or pole/residue formats not interchangeable between EDA tools
- Lowest common denominator – Berkeley SPICE RLC elements and controlled gain elements
- Implementation based on solving for poles and zeros and then cascading unit gain stages with efficient grouping.
- Automatic node numbering
- Stages referenced to one megohm ($M\Omega$) resistor



SPICE Macromodels

- G. Boyle, B. Cohn, D. Pederson, J. Solomon, “Macromodeling of Integrated Circuit Operational Amplifiers”, IEEE Journal of Solid-State Circuits, Vol. SC-9, No. 6, Dec. 1974, pp. 353-363
 - Dominant and second real pole
 - A commercial vendor macromodel adapted to illustrate a general behavioral macromodel generation strategy
 - Strategy can be applied to high-speed networks
- Cascaded SPICE elements are common practice from several vendors, but some macromodels use:
 - Real left-hand plane (LHP) poles and zeros
 - No right-hand plane (RHP) zeros
 - No complex poles or zeros
 - Extractions often based on frequency domain magnitude and phase measurements



Networks

- **Basic** Stages (simple poles and zeros or combinations)
- **Constructed** Stages (combining several basic networks for an overall set of poles and zeros)
- **Utility** Networks for pole/zero cancelation
- **All-pass** Networks for cancellations
- Efficiencies relative to a single-pole stage (combined P+Z stages usually more efficient)
 - Parts per pole+zero relative to **3.0**
 - Nodes per pole+zero relative to **1.0**



Basic Stages

BASIC STAGES:

| Real Zeros | Cmplx Conj Zeros | Real Poles | Cmplx Conj Poles | Poles+ Zeros | Stages | Parts | New Nodes | Parts Per P + Z | Nodes Per P + Z |
|------------|------------------|------------|------------------|--------------|--------|-------|-----------|-----------------|-----------------|
|------------|------------------|------------|------------------|--------------|--------|-------|-----------|-----------------|-----------------|

1. Real Pole

| | | | | | | | | | |
|--|--|---|--|---|---|---|---|---|---|
| | | X | | 1 | 1 | 3 | 1 | 3 | 1 |
|--|--|---|--|---|---|---|---|---|---|

2. Real Pole, Real Zero

2a. $z < p$ 2b. $z > p$

| | | | | | | | | | |
|---|--|---|--|---|---------|---|---|---|---|
| O | | X | | 2 | a, b: 1 | 4 | 2 | 2 | 1 |
|---|--|---|--|---|---------|---|---|---|---|

3. Complex-Conjugate Poles

| | | | | | | | | | |
|--|--|---|--|---|---|---|---|---|---|
| | | X | | 2 | 1 | 4 | 2 | 2 | 1 |
| | | X | | | | | | | |

4. Complex-Conjugate Poles, Real Zero

4a. $z < 2\sigma$ 4b. $z > (\omega^2 + \sigma^2) / 2\sigma$


| | | | | | | | | | |
|---|--|---|--|---|------|---|---|------|------|
| O | | X | | 3 | a: 1 | 5 | 2 | 1.67 | 0.67 |
| | | X | | | b: 1 | 5 | 3 | 1.67 | 1 |



Basic Stages

BASIC STAGES:

1. Real Pole

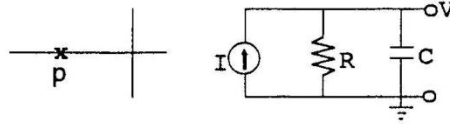


$$\frac{V}{I} = \frac{R}{(1 + s/p)}$$

$$C = 1/Rp$$

2. Real Pole, Real Zero

2a. ($z < p$)

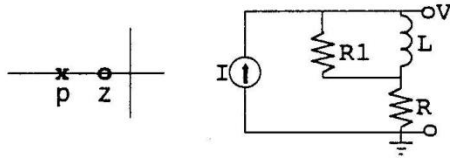


$$\frac{V}{I} = \frac{R(1 + s/z)}{(1 + s/p)}$$

$$R1 = R / (p/z - 1)$$

$$L = R1 / p$$


2b. ($z > p$)

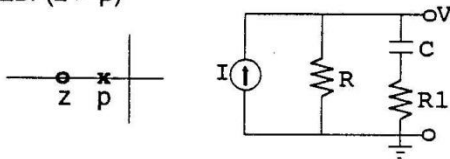

$$R1 = R / (z/p - 1)$$

$$C = 1/R1z$$

3. Complex-Conjugate Poles

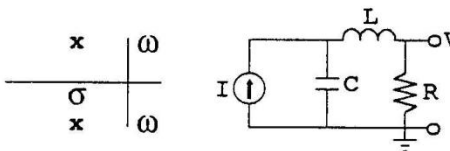

$$\frac{V}{I} = \frac{R}{(1 + 2\sigma s / (\omega^2 + \sigma^2) + s^2 / (\omega^2 + \sigma^2))}$$

$$L = R / 2\sigma$$


$$C = 1 / L(\omega^2 + \sigma^2)$$



Basic Stages (Continued)

4. Complex-Conjugate Poles, Real Zero

4a. ($z < 2\sigma$)

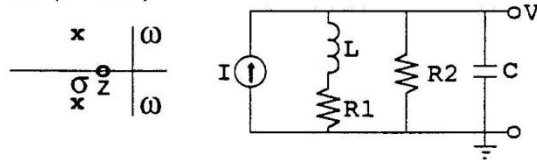

$$\frac{V}{I} = \frac{R(1 + s/z)}{(1 + 2\sigma s / (\omega^2 + \sigma^2) + s^2 / (\omega^2 + \sigma^2))}$$


$$C = z / R (\omega^2 + \sigma^2)$$

$$R2 = 1 / C (2\sigma - z)$$

$$R1 = R R2 / (R2 - R)$$

$$L = R1 / z$$

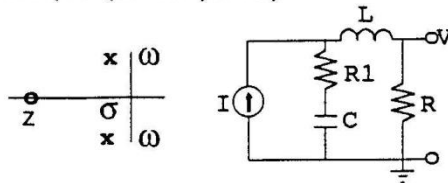4b. ($z > (\omega^2 + \sigma^2) / 2\sigma$)



$$C = (2\sigma / (\omega^2 + \sigma^2) - 1/z) / R$$

$$R1 = 1 / C z$$

$$L = 1 / C (\omega^2 + \sigma^2)$$

Constructed Stages

CONSTRUCTED STAGES:

| Real Zeros | Cmplx Conj Zeros | Real Poles | Cmplx Conj Poles | Poles+ Zeros | Stages | Parts | New Nodes | Parts Per P + Z | Nodes Per P + Z |
|------------|------------------|------------|------------------|--------------|--------|-------|-----------|-----------------|-----------------|
|------------|------------------|------------|------------------|--------------|--------|-------|-----------|-----------------|-----------------|

4. Complex-Conjugate Poles, Real Zero (10 & 2)

$$4c. (\omega^2 + \sigma^2) / 2\sigma > Z > 2\sigma$$

| | | | | | | | | | |
|---|--|--|--------|---|------|---|---|------|------|
| O | | | X X | 3 | c: 2 | 8 | 4 | 2.67 | 1.33 |
|---|--|--|--------|---|------|---|---|------|------|

5. Complex-Conjugate Poles, Two Real Zeros (11 & 2)

| | | | | | | | | | |
|-----|--|--|--------|---|-------------|---------|--------|--------------|--------------|
| O O | | | X X | 4 | 2 max: 3 | 9 13 | 5 7 | 2.25 3.25 | 1.25 1.75 |
|-----|--|--|--------|---|-------------|---------|--------|--------------|--------------|

6. Complex-Conjugate Poles, Complex-Conjugate Zeros (11, 12 & 2)

| | | | | | | | | | |
|--|--------|--|--------|---|---|----|---|-----|------|
| | O O | | X X | 4 | 3 | 14 | 7 | 3.5 | 1.75 |
|--|--------|--|--------|---|---|----|---|-----|------|

7. Two Real Poles, Complex-Conjugate Zeros (12 & 2)

| | | | | | | | | | |
|--|--------|-----|--|---|-------------|---------|--------|--------------|----------|
| | O O | X X | | 4 | 2 max: 3 | 9 13 | 4 6 | 2.25 3.25 | 1 1.5 |
|--|--------|-----|--|---|-------------|---------|--------|--------------|----------|

8. Complex-Conjugate Poles, Real Pole, Complex-Conjugate Zeros (12 & 4)

| | | | | | | | | | |
|--|--------|---|--------|---|-----------------------|----------------|-------------|---------------|-----------------|
| | O O | X | X X | 5 | min: 2 2 max: 4 | 10 10 17 | 5 6 8 | 2 2 3.4 | 1 1.2 1.6 |
|--|--------|---|--------|---|-----------------------|----------------|-------------|---------------|-----------------|

9. Complex-Conjugate Poles Real Pole, Complex-Conjugate Zeros, Real Zero (11, 12 & 2)

| | | | | | | | | | |
|---|--------|---|--------|---|-------------|----------|---------|--------------|--------------|
| O | O O | X | X X | 6 | 3 max: 5 | 14 22 | 7 11 | 2.33 3.67 | 1.14 1.83 |
|---|--------|---|--------|---|-------------|----------|---------|--------------|--------------|



Utility Networks and Combinations for Construction

UTILITY NETWORKS AND COMBINATIONS FOR CONSTRUCTION:

| Real Zeros | Cmplx Conj Zeros | Real Poles | Cmplx Conj Poles | Poles+ Zeros | Stages | Parts | New Nodes | Parts Per P + Z | Nodes Per P + Z |
|------------|------------------|------------|------------------|--------------|--------|-------|-----------|-----------------|-----------------|
|------------|------------------|------------|------------------|--------------|--------|-------|-----------|-----------------|-----------------|

10. Complex-Conjugate Poles, Fixed Real Zero

| | | | | | | | | | |
|--------------|--|--|--------|---|---|---|---|------|------|
| O ^ fixed | | | X X | 3 | 1 | 4 | 2 | 1.33 | 0.67 |
|--------------|--|--|--------|---|---|---|---|------|------|

11. Complex-Conjugate Poles, Real Zero, Fixed Real Zero

11a. $Z < 2\sigma$ 11b. $Z > (\omega^2 + \sigma^2) / 2\sigma$ 11c. $(\omega^2 + \sigma^2) / 2\sigma > Z > 2\sigma$ (by combination of 11a & 2)

| | | | | | | | | | |
|----------------|--|--|--------|---|----------------------|-------------|-------------|----------------------|----------------------|
| OO ^or^ fix | | | X X | 4 | a: 1 b: 1 c: 2 | 5 5 9 | 3 3 5 | 1.25 1.25 2.25 | 0.75 0.75 1.25 |
|----------------|--|--|--------|---|----------------------|-------------|-------------|----------------------|----------------------|

12. Complex-Conjugate Zeros, Real Pole, Fixed Real Pole

12a. $p < 2\sigma$ 12b. $p > (\omega^2 + \sigma^2) / 2\sigma$ 12c. $(\omega^2 + \sigma^2) / 2\sigma > p > 2\sigma$ (by combination of 12a & 2)



| | | | | | | | | | |
|--|--------|-----------------|--|---|----------------------|-------------|-------------|----------------------|-----------------|
| | O O | X X ^or^ fix | | 4 | a: 1 b: 1 c: 2 | 5 5 9 | 2 2 4 | 1.25 1.25 2.25 | 0.5 0.5 1 |
|--|--------|-----------------|--|---|----------------------|-------------|-------------|----------------------|-----------------|



Utility Networks for Construction

UTILITY NETWORKS FOR CONSTRUCTION:

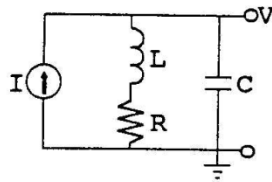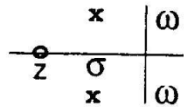10. Complex-Conjugate Poles, Fixed Real Zero



$$\frac{V}{I} = \frac{R(1 + s/z)}{(1 + 2\sigma s / (\omega^2 + \sigma^2) + s^2 / (\omega^2 + \sigma^2))}$$

$$L = R / 2\sigma$$


$$C = 1 / L (\omega^2 + \sigma^2)$$

$$z = 2\sigma$$



Utility Networks (Continued)

11. Complex-Conjugate Poles, Real Zero, Fixed Real Zero

11a. ($z_1 < 2\sigma$)

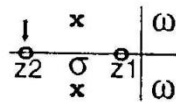

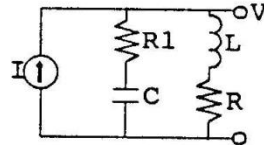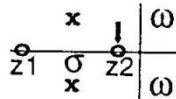11b. ($z_1 > (\omega^2 + \sigma^2) / 2\sigma$)



$$\frac{V}{I} = \frac{R(1 + s/z_1)(1 + s/z_2)}{(1 + 2\sigma s / (\omega^2 + \sigma^2) + s^2 / (\omega^2 + \sigma^2))}$$

$$L = R / z_1$$

$$C = 1 / L (\omega^2 + \sigma^2)$$

$$R_1 = R / (2\sigma / z_1 - 1)$$

$$z_2 = 1 / R_1 C$$

$$C = (2\sigma / (\omega^2 + \sigma^2) - 1 / z_1) / R$$


$$R_1 = 1 / C z_1$$

$$L = 1 / C (\omega^2 + \sigma^2)$$



$$z_2 = R / L$$

12. Complex-Conjugate Zeros, Real Pole

12a. ($p_1 < 2\sigma$)

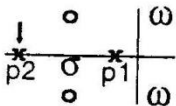

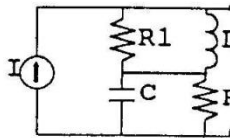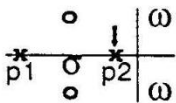12b. ($p_1 > (\omega^2 + \sigma^2) / 2\sigma$)



$$\frac{V}{I} = \frac{R(1 + 2\sigma s / (\omega^2 + \sigma^2) + s^2 / (\omega^2 + \sigma^2))}{(1 + s/p_1)(1 + s/p_2)}$$

$$C = 1 / R p_1$$

$$L = 1 / C (\omega^2 + \sigma^2)$$

$$R_1 = R / (2\sigma / p_1 - 1)$$

$$p_2 = R_1 / L$$

$$C = 1 / L (\omega^2 + \sigma^2)$$

$$L = R (2\sigma / (\omega^2 + \sigma^2) - 1 / p_1)$$

$$R_1 = L / p_1$$


$$p_2 = 1 / RC$$



All-Pass Networks (Mirrored P/Z)

ALL-PASS NETWORKS FOR RIGHT-HAND PLANE ZEROS (WITH MIRRORED POLES):

13. RHP Real Zero, Fixed Real Pole

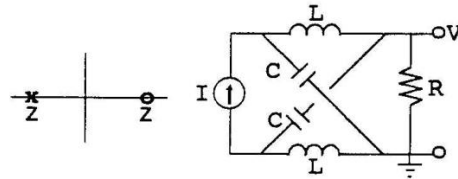


$$\frac{V}{I} = \frac{R(1 - s/z)}{(1 + s/z)}$$

$$L = R/z$$

$$C = 1/R^2$$

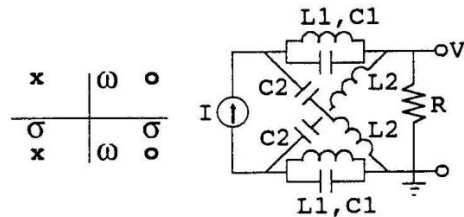14. RHP Complex-Conjugate Zeros, Fixed Complex-Conjugate Poles



$$\frac{V}{I} = \frac{R(1 - 2\sigma s / (\omega^2 + \sigma^2) + s^2 / (\omega^2 + \sigma^2))}{(1 + 2\sigma s / (\omega^2 + \sigma^2) + s^2 / (\omega^2 + \sigma^2))}$$

$$C1 = 1 / 2R \sigma$$

$$L1 = 1 / C1 (\omega^2 + \sigma^2)$$

$$L2 = R^2 C1$$

$$C2 = 1 / L2 (\omega^2 + \sigma^2)$$

ALL-PASS NETWORKS FOR RIGHT HAND PLANE ZEROS (WITH MIRRORED POLES):

| Real Zeros | Cmplx Conj Zeros | Real Poles | Cmplx Conj Poles | Poles+ Zeros | Stages | Parts | New Nodes | Parts Per P + Z | Nodes Per P + Z |
|------------|------------------|------------|------------------|--------------|--------|-------|-----------|-----------------|-----------------|
|------------|------------------|------------|------------------|--------------|--------|-------|-----------|-----------------|-----------------|

13. RHP Real Zero, Fixed Real Pole


| | | | | | | | | | |
|-------|--|--------------|--|---|---|---|---|---|-----|
| RHP O | | X ^ fixed | | 2 | 1 | 6 | 3 | 3 | 1.5 |
|-------|--|--------------|--|---|---|---|---|---|-----|

14. RHP Complex-Conjugate Zeros, Fixed Complex-Conjugate Poles

| | | | | | | | | | |
|--|-------|--|---------|---|---|----|---|-----|------|
| | RHP O | | X fixed | 4 | 1 | 10 | 5 | 2.5 | 1.25 |
| | RHP O | | X fixed | | | | | | |



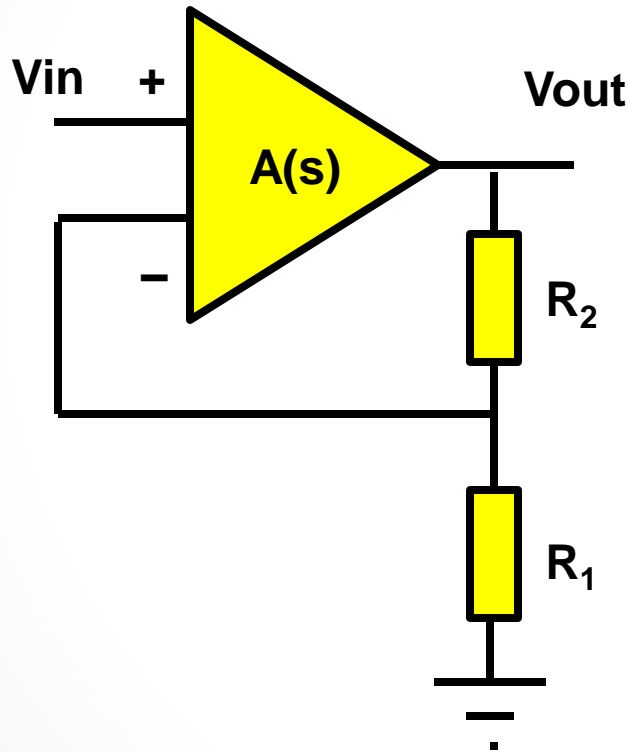Open Loop (OL) AC Model from Closed Loop (CL) Response



Extracted $H(s) = V_{out}/V_{in}$ from
time response = $N(s)/D(s)$

$$G = (R_1 + R_2)/R_1$$

$$H(s) = A(s)/[1 + A(s)/G]$$

$$A(s) = H(s) + H(s)A(s)/G$$


$$A(s) = H(s)/[1 - H(s)/G]$$

$$A(s) = [N(s)/D(s)]/[1 - N(s)/GD(s)]$$

$$A(s) = N(s)/[D(s) - N(s)/G]$$

Poles and zeros of $A(s)$ produces
OL AC Model

Operational Amplifier AC Model Example

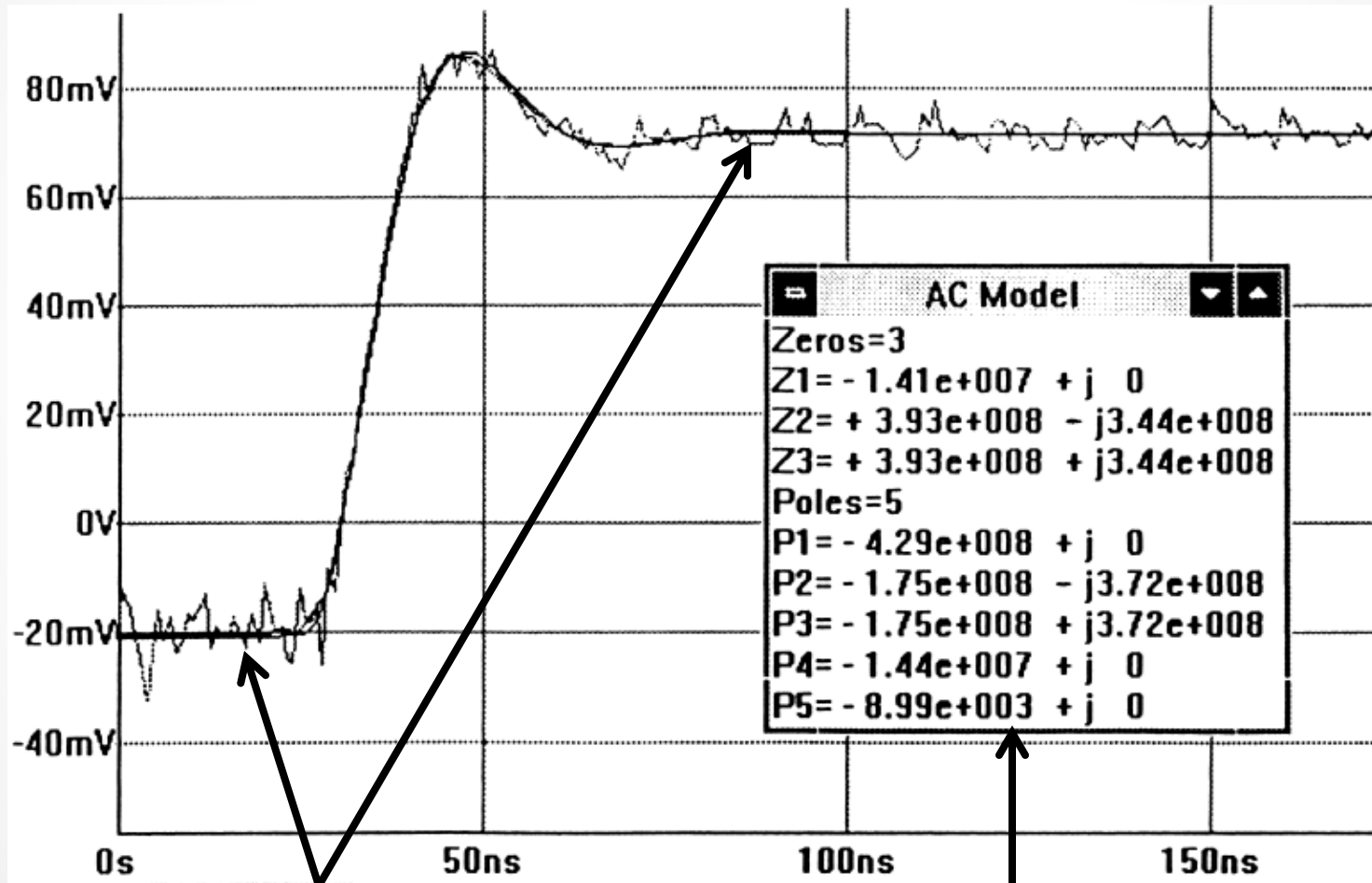

Closed Loop Samples
and Response

Open Loop Poles and Zeros



Generated SPICE Macromodel

```

AC Model
Zeros=3
Z1= -1.41e+007 + j 0
Z2= + 3.93e+008 - j3.44e+008
Z3= + 3.93e+008 + j3.44e+008
Poles=5
P1= -4.29e+008 + j 0
P2= -1.75e+008 - j3.72e+008
P3= -1.75e+008 + j3.72e+008
P4= -1.44e+007 + j 0
P5= -8.99e+003 + j 0
    
```

Poles and zeros shown in radians and MHz in the macromodel

```

*
* SETUP PARAMETERS
* NPN Bipolar Junction Transistor Input
* Vcc = 15 V, Vee = -15 V
* Input Stage Tail Current = 0.1 mA
*
* MEASURED (OR USER OVERRIDDEN) PARAMETERS
*
* Srp = 135.3 V/us, Srn = 135.3 V/us
* Avd = 94.211 dB at RL(Load) = 1e+009 kohms
* f(0dB) = 71.8 MHz, Phi(Phase Margin) = 222.2 deg
    
```

| ZEROS | | Radians | | MHz | |
|------------|------------|------------|------------|----------|-----------|
| Real | Imaginary | Real | Imaginary | Real | Imaginary |
| -1.41e+007 | 0 | -1.41e+007 | 0 | -2.24408 | 0 |
| 3.93e+008 | -3.44e+008 | 3.93e+008 | -3.44e+008 | 62.5479 | -54.7493 |
| 3.93e+008 | 3.44e+008 | 3.93e+008 | 3.44e+008 | 62.5479 | 54.7493 |

| POLES | | Radians | | MHz | |
|------------|------------|------------|------------|------------|-----------|
| Real | Imaginary | Real | Imaginary | Real | Imaginary |
| -8990 | 0 | -8990 | 0 | -0.0014308 | 0 |
| -1.44e+007 | 0 | -1.44e+007 | 0 | -2.29183 | 0 |
| -1.75e+008 | -3.72e+008 | -1.75e+008 | -3.72e+008 | -27.8521 | -59.2056 |
| -1.75e+008 | 3.72e+008 | -1.75e+008 | 3.72e+008 | -27.8521 | 59.2056 |
| -4.29e+008 | 0 | -4.29e+008 | 0 | -68.2775 | 0 |

```

*
* NON-INVERTING INPUT
* INVERTING INPUT
* POSITIVE POWER SUPPLY
* NEGATIVE POWER SUPPLY
* OUTPUT
*
.SUBCKT OPamp 1 2 99 50 52
*
* INPUT STAGE (NO POLE)
*
R1 2 3 5e+011
R2 1 3 5e+011
R3 5 99 2930.88
R4 6 99 2930.88
I1 4 50 0.0001
IOS 1 2 1.095e-009
EOS 9 1 POLY(1) 59 49 -0.001136 1
Q1 5 2 7 QX
Q2 6 9 8 QX
R5 4 7 2421.07
R6 4 8 2421.07
*
EREF 98 0 49 0 1
*
    
```



Low Frequency Pole

EREF 98 0 49 0 1

* SECOND STAGE POLE AT 1430.8 HZ

R21 100 98 1.50501e+008
 C21 100 98 7.39098e-013
 G21 100 98 6 5 0.000341195
 V21 99 21 2.39393
 V22 22 50 2.41393
 D21 100 21 DX
 D22 22 100 DX

* RHP COMPLEX ZEROS AT 62.5479 +/- j 54.7493 MHZ
 * NEW LHP COMPLEX POLES AT 62.5479 +/- j 54.7493 MHZ

R101 105 98 1e+006
 C101 101 98 1.27226e-015
 C102 105 102 1.27226e-015
 C103 105 103 2.88139e-015
 C104 104 98 2.88139e-015
 L101 101 98 0.00288139
 L102 105 102 0.00288139
 L103 101 103 0.00127226
 L104 102 104 0.00127226
 G101 102 101 49 100 1e-006

| | Real | Imaginary |
|--|----------|-----------|
| | -2.24408 | 0 |
| | 62.5479 | -54.7493 |
| | 62.5479 | 54.7493 |

| | Real | Imaginary |
|--|------------|-----------|
| | -0.0014308 | 0 |
| | -2.29183 | 0 |
| | -27.8521 | -59.2056 |
| | -27.8521 | 59.2056 |
| | -68.2775 | 0 |

***** CONSTRUCTED STAGE *****

* LHP REAL ZERO AT 2.24408 MHZ
 * LHP COMPLEX ZEROS AT 62.5479 +/- j 54.7493 MHZ
 * LHP REAL POLE AT 2.29183 MHZ
 * LHP COMPLEX POLES AT 27.8521 +/- j 59.2056 MHZ

* LHP ZERO AT 2.24408 MHZ
 * NEW LHP ZERO AT 80.0792 MHZ
 * LHP COMPLEX POLES AT 27.8521 +/- j 59.2056 MHZ

R106 108 106 1e+006
 R107 108 107 2.38227e+007
 C106 107 98 8.34275e-017
 L106 106 98 0.070922
 G106 108 98 49 105 1e-006

* LHP COMPLEX ZEROS AT 62.5479 +/- j 54.7493 MHZ
 * LHP POLE AT 2.29183 MHZ
 * NEW LHP POLE AT 56.2663 MHZ

R109 110 109 1e+006
 R110 109 98 18662.5
 C109 110 109 6.94444e-014
 L109 109 98 5.27888e-005
 G109 110 98 49 108 1e-006

* LHP ZERO AT 56.2663 MHZ
 * LHP POLE AT 80.0792 MHZ

R111 112 111 1e+006
 R112 111 98 423218
 L111 111 98 0.000841133
 G111 112 98 49 110 1e-006

***** END OF CONSTRUCTED STAGE *****



3 Poles, 3 Zeros using Cancellations

```

-
EREF 98 0 49 0 1
*
* SECOND STAGE POLE AT 1430.8 HZ
*
R21 100 98 1.50501e+008
C21 100 98 7.39098e-013
G21 100 98 6 5 0.000341195
V21 99 21 2.39393
V22 22 50 2.41393
D21 100 21 DX
D22 22 100 DX
    
```

```

* RHP COMPLEX ZEROS AT 62.5479 +/- j 54.7493 MHZ
* NEW LHP COMPLEX POLES AT 62.5479 +/- j 54.7493 MHZ
    
```

```

R101 105 98 1e+006
C101 101 98 1.27226e-015
C102 105 102 1.27226e-015
C103 105 103 2.88139e-015
C104 104 98 2.88139e-015
L101 101 98 0.00288139
L102 105 102 0.00288139
L103 101 103 0.00127226
L104 102 104 0.00127226
G101 102 101 49 100 1e-006
*
    
```

Cancellation

(9)

(14)

| | Real | Imaginary |
|-----|----------|-----------|
| MHz | -2.24408 | 0 |
| | 62.5479 | -54.7493 |
| | 62.5479 | 54.7493 |

| | Real | Imaginary |
|-----|------------|-----------|
| MHz | -0.0014308 | 0 |
| | -2.29183 | 0 |
| | -27.8521 | -59.2056 |
| | -27.8521 | 59.2056 |
| | -68.2775 | 0 |

***** CONSTRUCTED STAGE *****

```

* LHP REAL ZERO AT 2.24408 MHZ
* LHP COMPLEX ZEROS AT 62.5479 +/- j 54.7493 MHZ
* LHP REAL POLE AT 2.29183 MHZ
* LHP COMPLEX POLES AT 27.8521 +/- j 59.2056 MHZ
    
```

```

* LHP ZERO AT 2.24408 MHZ
* NEW LHP ZERO AT 80.0792 MHZ
* LHP COMPLEX POLES AT 27.8521 +/- j 59.2056 MHZ
    
```

```

R106 108 106 1e+006
R107 108 107 2.38227e+007
C106 107 98 8.34275e-017
L106 106 98 0.070922
G106 108 98 49 105 1e-006
    
```

```

* LHP COMPLEX ZEROS AT 62.5479 +/- j 54.7493 MHZ
* LHP POLE AT 2.29183 MHZ
* NEW LHP POLE AT 56.2663 MHZ
    
```

```

R109 110 109 1e+006
R110 109 98 18662.5
C109 110 109 6.94444e-014
L109 109 98 5.27888e-005
G109 110 98 49 108 1e-006
    
```

```

* LHP ZERO AT 56.2663 MHZ
* LHP POLE AT 80.0792 MHZ
    
```

```

R111 112 111 1e+006
R112 111 98 423218
L111 111 98 0.000841133
G111 112 98 49 110 1e-006
    
```

***** END OF CONSTRUCTED STAGE *****

(11)

(12)

(2)

Cancellations



Last Pole and Last Stages

```

MHz
Real      Imaginary
-2.24408  0
62.5479   -54.7493
62.5479    54.7493
    
```

```

MHz
Real      Imaginary
-0.0014308  0
-2.29183    0
-27.8521    -59.2056
-27.8521    59.2056
-68.2775    0
    
```

* LHP POLE AT 68.2775 MHZ

(1)

```

R113  113  98  1e+006
C113  113  98  2.331e-015
G113  113  98  49  112  1e-006
*
* COMMON MODE GAIN STAGE WITH ZERO AT 20 KHZ
*
R57   59   57  1e+006
C57   59   57  7.95775e-012
R58   59   98  1
E57   57   98  49  3  3.55745
*
    
```

```

* OUTPUT STAGE
*
R49   49   99  18005
R50   49   50  18005
ISY   99   50  0.0058135
R61   60   99  73.2
R62   60   50  73.2
L61   60   52  1e-012
G63   63   50  113  60  0.0136612
G64   64   50  60  113  0.0136612
G65   60   99  99  113  0.0136612
G66   50   60  113  50  0.0136612
V61   61   60  3.38846
V62   60   62  3.38846
D61   113  61  DX
D62   62  113  DX
D63   99  63  DX
D64   99  64  DX
D65   50  63  DY
D66   50  64  DY
*
* MODELS AND END
*
.MODEL QX NPN(IS=1e-015 BF=2076)
.MODEL DX D(IS=1e-015)
.MODEL DY D(IS=1e-015 BV=50)
.ENDS
    
```




Build Strategy Demonstrated

- Sort (by magnitude) poles and zeros in four bins:
 - **Real poles** (lowest may be in early stage of operational amplifier)
 - **Complex-conjugate poles**
 - **Real zeros**
 - **Complex-conjugate zeros**
- Model complex-conjugate RHP zeros by all-pass network 14 or real RHP zeros by 13 and then in priority order use 9, 8, 7, and 6
- Model real zeros in priority order 5, 4, and 2
- Model remaining poles by 3 and 1
- Apply pole/zero cancellation for any “new” or “fixed” poles or zeros



Frequency Plots from Laplace Transform

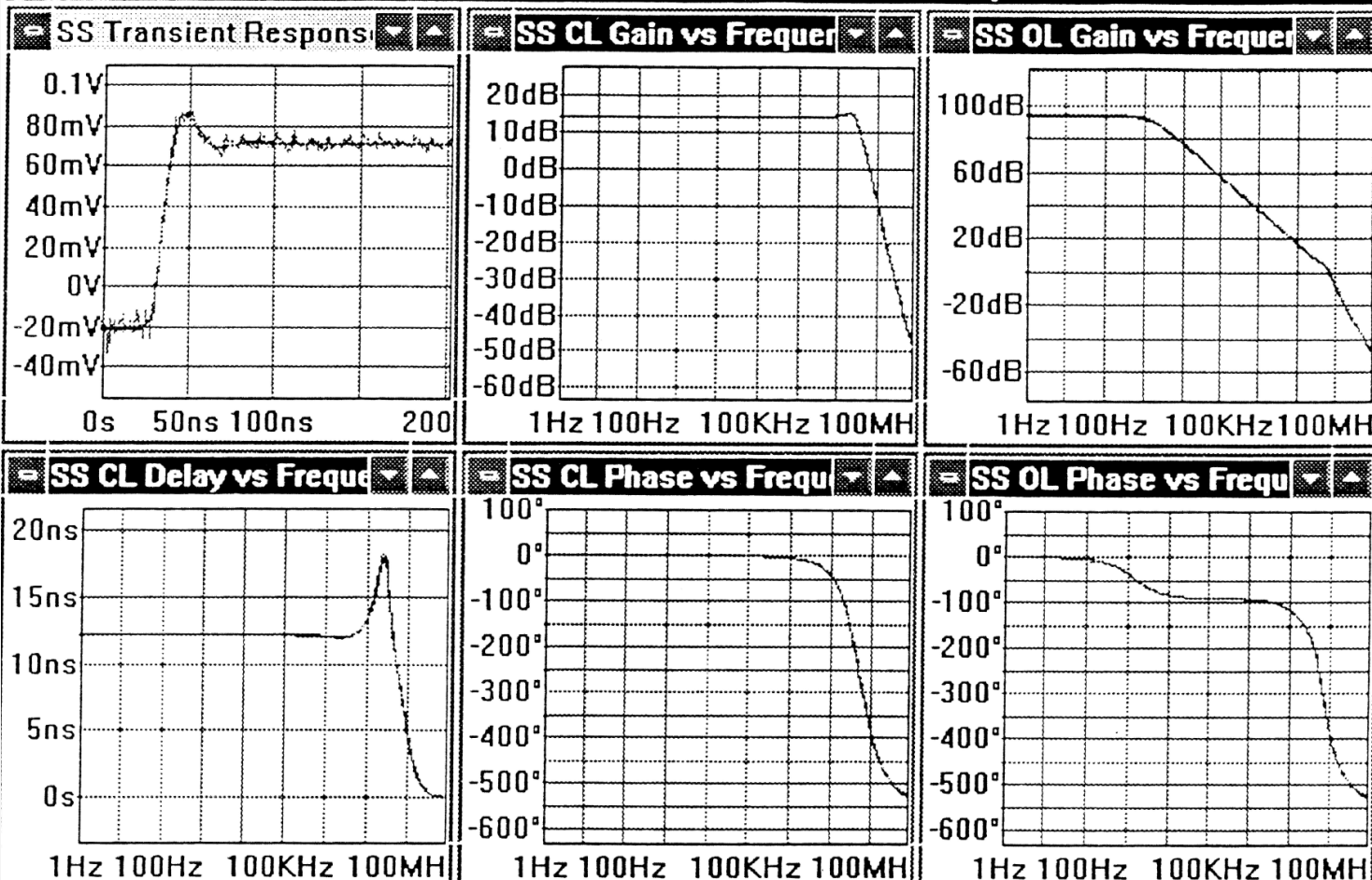

“SS” is small signal

Conclusion

- **SPICE macromodel generation strategy uses unity gain, cascaded RLC pole and zero stages**
- **Pole/zero cancellation is effective for adding RHP zeros**
- **Operational amplifier macromodel illustrates the process**
- **Process can be applied to any macromodel including those for high-speed applications**

